

Does a lamp add energy to or remove energy from a circuit?