



The voltage across the lamp is 2V. The power is 8W.
What is the current running through the lamp?