

The current through lamp B is 2A. The current through lamp C is 3A. What is the current at point A?