

The current at point D is 3A. What is the current at point A?