

For electricity to flow, there must be a continuous loop.  
This loop is called a.....