

The current at point A is 5A. The current through lamp B is 2.5A. What is the current through lamp C, in amps?