



The voltage across the cell (A) is 3V. The voltage across lamp B is 3V. What is the voltage across lamp C?