



The voltage increase across the cell (A) is 3V. What is the voltage decrease across the lamp (B)?