



The voltage across the lamp is 6V. The power is 12W.
What is the current running through the lamp?