



The current through the ammeter is 1A. The resistance of the lamp is 3Ω . What is the voltage across the lamp?