



The current through lamp B is 0.5A . The current through lamp C is 1.5A . What is the current at point D?