



The current through the ammeter is  $0.5\text{A}$ . The voltage across the lamp is  $3\text{V}$ . What is the resistance of the lamp, in ohms?