

The current at point A is 5A. What is the current at point D?