

The current at point A is 2A. The current through lamp B is 1.5A. What is the current through lamp C, in amps?