

Does a cell add energy to or remove energy from a circuit?