



The voltage increase across the cell (A) is  $1.2\text{V}$ . What is the voltage decrease across the lamp?