

The voltage increase across the cells (A) is 12V. The voltage decrease across the first lamp (B) is 3V. What is the voltage decrease across the second lamp (C)?