



The current through the ammeter is 1A. The resistance of the lamp is  $3\Omega$ . What is the voltage across the lamp?