



The voltage increase across the cell (A) is 1.2V . What is the voltage decrease across the lamp?