

If we add an extra cell to a series circuit, in the same direction as the existing cell(s), what will happen to the current?