

An electric blanket uses 240W at 240V. What is the current running through it?