



The current through the ammeter is 4A . The resistance of the lamp is 2Ω . What is the voltage across the lamp?