

All components in a circuit resist the flow of current through them. The lower the resistance the bigger the current that flows through.