



The current through the ammeter is 3A. The voltage across the lamp is 6V. What is the resistance of the lamp, in ohms?