



The current through the ammeter is 2A. The voltage across the lamp is 3V. What is the resistance of the lamp, in ohms?