



The voltage across the lamp is 2V. The resistance of the lamp is 4Ω . What is the current through the lamp?