



The current through the ammeter is 0.5A . The voltage across the lamp is 2V . What is the resistance of the lamp, in ohms?