



The current through the ammeter is  $2\text{A}$ . The resistance of the lamp is  $3\Omega$ . What is the voltage across the lamp?