



The voltage across the lamp is 1.5V. The current through the lamp is 4A. How much electrical power is the lamp using, in watts?