

The voltage across the cell (A) is 6V. The voltage across lamp B is 6V. What is the voltage across lamp C?