

Does an LED (light emitting diode) add energy to or remove energy from a circuit?