

If we add an extra resistor to a series circuit, what will happen to the current?