



The voltage increase across the cells (A) is 3V. The voltage decrease across the first lamp (B) is 2V. What is the voltage decrease across the second lamp (C)?