



The voltage across the cell (A) is 8V. The voltage across lamp B is 8V. What is the voltage across lamp C?