

The voltage increase across the cells (A) is 3V. The voltage decrease across the first lamp (B) is 1.5V. What is the voltage decrease across the second lamp (C), in volts?