



The voltage across the cell (A) is 1.5V. What is the voltage across lamp B?