



The voltage across the lamp is 2V. The resistance of the lamp is  $4\Omega$ . What is the current through the lamp?