A circuit with two or more one paths for electricity to flow is called a ...... circuit.